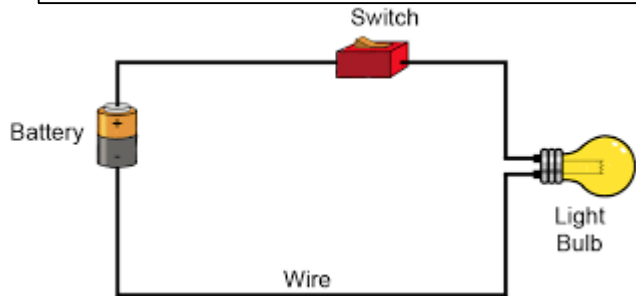


# Summer Term Year Three

## Science: Electricity

### You should be able to....

- Identify common appliances that run on electricity.
- Construct a simple series electrical circuit, identifying and naming its basic parts, including cells, wires, bulbs, switches and buzzers.
- Identify whether or not a lamp will light in a simple series circuit, based on whether or not the lamp is part of a complete loop with a battery.
- Recognise that a switch opens and closes a circuit and associate this with whether or not a lamp lights in a simple series circuit.
- Recognise some common conductors and insulators, and associate metals with being good conductors.




**Electricity** can only flow around a complete **circuit** that has no gaps. There must be wires connected to both the positive and negative end of the **power supply/battery**.
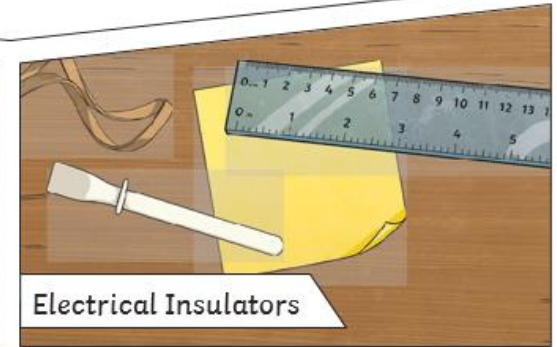
### Key vocabulary:

Electricity, electrical appliance/device, mains, plug, electrical circuit, complete circuit, component, cell, battery, positive, negative, connect/connections, loose connection, short circuit, crocodile clip, bulb, switch, buzzer, motor, conductor, insulator, metal, non-metal, symbol.

A conductor of **electricity** is a material that will allow **electricity** to flow through it. Metals are good conductors. Materials that are electrical insulators do not allow **electricity** to flow through them. Wood, plastic and glass are good insulators



Many everyday **appliances** rely on **electricity** for them to work. Some appliances use mains **electricity** (are plugged into a socket) and others have a **battery** to make them work.



Switches can be used to open or close a **circuit**. When off, a switch 'breaks' the **circuit** to stop the flow of **electricity**. When on, a switch 'completes' the circuit and allows the **electricity** to flow.

